

## 5.2.2 Dice Game



### Problem description



- Design an electronic dice game involves 2 dice, each of which can have a value 1 ~ 6.
  - Two counters are used to simulate the roll of the dice.
    - Each counter counts in the sequence 1, 2, 3, 4, 5, 6, 1, 2, ....
    - After the “roll” of the dice, the sum of the values in the two counters will be in the range 2 through 12.

5-38



### Rules of the game:

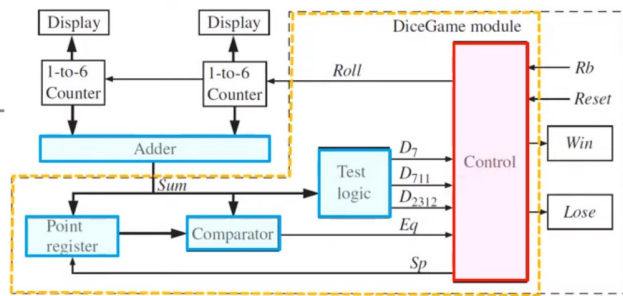
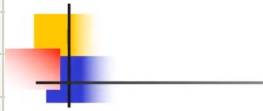
1. After the **first roll** of the dice, the player wins if the sum is 7 or 11. The player loses if the sum is 2, 3, or 12. Otherwise, the sum the player obtained on the first roll is a point, and he/she must roll again.
2. On the **second or next roll** of the dice, the player wins if the sum equals the point, and he/she loses if the sum is 7. Otherwise, the player must roll again until he/she finally wins or loses.



### ■ Input signals to the control ckt:

- ***Rb*** = 1 when the roll button is pressed.
- ***Reset*** = 1 when the reset button is pressed.
- ***D<sub>7</sub>*** = 1 if the sum of the dice is 7
- ***D<sub>711</sub>*** = 1 if the sum of the dice is 7 or 11
- ***D<sub>2312</sub>*** = 1 if the sum of the dice is 2, 3, or 12
- ***Eq*** = 1 if the sum of the dice equals the number stored in the point register

J.J. Shann 5-42

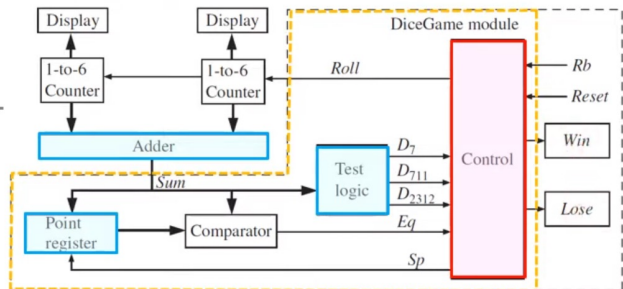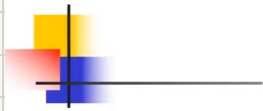

### ■ Outputs from the control ckt:

- ***Roll*** = 1 enables the dice counters.
- ***Sp*** = 1 stores the sum into the point register.
- ***Win*** = 1 turns on the win light.
- ***Lose*** = 1 turns on the lose light.

J.J. Shann 5-43

# Flowchart

## Input signals to the control ckt:


- $Rb$  = 1 when the roll button is pressed.
- $Reset$  = 1 when the reset button is pressed.
- $D_7$  = 1 if the sum of the dice is 7
- $D_{711}$  = 1 if the sum of the dice is 7 or 11
- $D_{2312}$  = 1 if the sum of the dice is 2, 3, 12
- $Eq$  = 1 if the sum of the dice equals the # stored in the point register

## Outputs from the control ckt:

- $Roll$  = 1 enables the dice counters.
- $Sp$  = 1 stores the into the point reg.
- $Win$  = 1 turns on the win light.
- $Lose$  = 1 turns on the lose light.
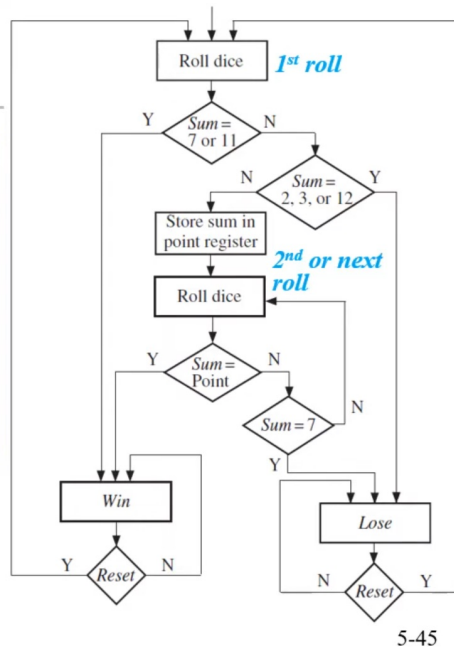
## \* Assumption:



The push buttons are properly debounced and the changes in  $Rb$  are properly synchronized w/ the clock.



5-45

# SM Chart

## Conversion of flowchart to SM chart:

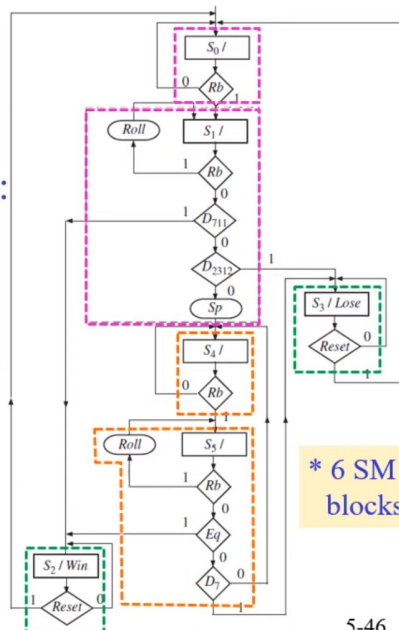
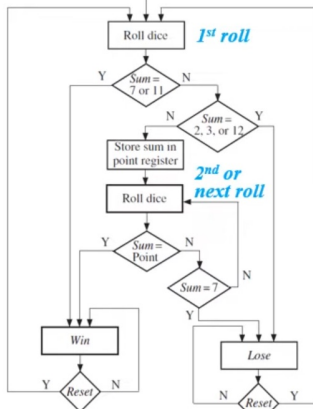


\* 6 SM blocks.

5-46
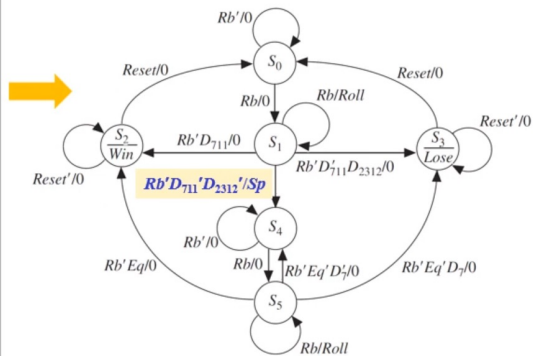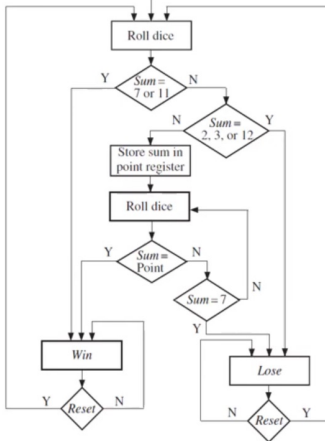
# State Graph


- Constructing an equivalent *state graph* from the flowchart: an alternative of using *SM chart*



5-47

# Testing

- Test the behavioral model:

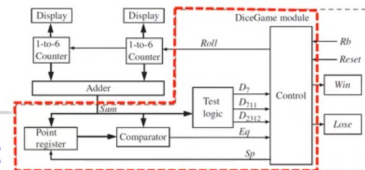

- Design a Verilog test bench module (GameTest) to *monitor* the *output signals* from the dice-game module and *supply* a sequence of *inputs* in response.
- Functions of the GameTest module :
  - Initially supply the *Rb* signal.
  - When the DiceGame responds with a *Roll* signal, supply a *Sum* signal, which represents the sum of the two dice.
  - If no *Win* or *Lose* signal is generated by the DiceGame, repeat steps 1 and 2 to roll again.
  - When a *Win* or *Lose* signal is detected, generate a *Reset* signal and start again.

5-60



## SM Chart of GameTest Module

- SM chart for the GameTest module:

