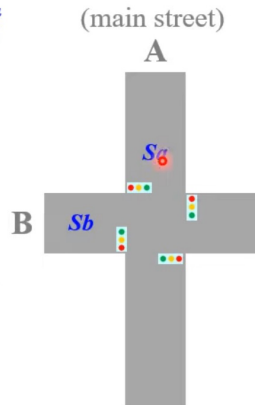


# 4.4 Traffic Light Controller

## Traffic Light Controller


### ■ Problem description: a *seq ckt*

- Design a traffic light controller for the intersection of street “A” and street “B”.
- Each street has traffic sensors, which detect the presence of vehicles approaching or stopped at the intersection.
  - $S_a = 1$ : a vehicle is approaching on street “A”
  - $S_b = 1$ : a vehicle is approaching on street “B”




J.J. Shann 4-35

- Street “A” is a main street.
- When “A” is green, it remains green at least 60 seconds.
- If there is no car approaches on “B”, the “A” cycle is extended for 10 additional seconds until a car approaches on “B”.
- Then the lights change, and “B” has a green light.
- At the end of 50 seconds, the lights change back to “A” unless there is a car on street “B” and none on “A”, in which case the “B” cycle is extended for 10 additional seconds.
- If cars continue to arrive on street “B” and no car appears on street “A”, “B” continues to have a green light.
- The yellow light lasts for 10 seconds.

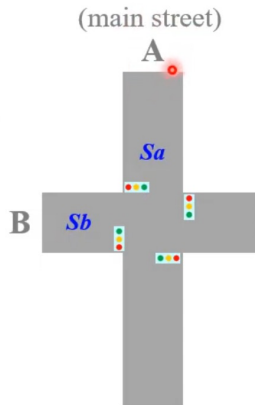


J.J. Shann 4-36

# Implementation :

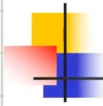
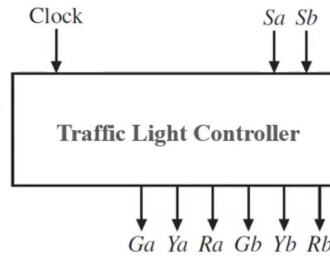
## Block Diagram

- Block diagram of traffic light controller:



– Inputs:

- $Sa = 1$  means a vehicle is approaching on street “A”
- $Sb = 1$  means a vehicle is approaching on street “B”

– Outputs:

- $Ga, Ya, Ra$ : drive the green, yellow, and red lights on street “A”
- $Gb, Yb, Rb$ : drive the corresponding lights on street “B”

J.J. Shann 4-37




## State Graph


- Moore State graph

– For timing purpose by a clock w/ a

- When “A” is green, it remains green at least 60 seconds.
- If there is no car approaches on “B”, the “A” cycle is extended for 10 additional seconds until a car approaches on “B”.
- Then the lights change, and “B” has a green light.
- At the end of 50 seconds, the lights change back to “A” unless there is a car on street “B” and none on “A”, in which case the “B” cycle is extended for 10 additional seconds.
- The yellow light lasts for 10 seconds.

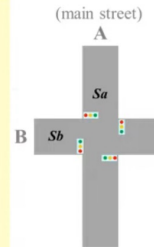

$$\frac{S_{13} \sim 16}{0}$$

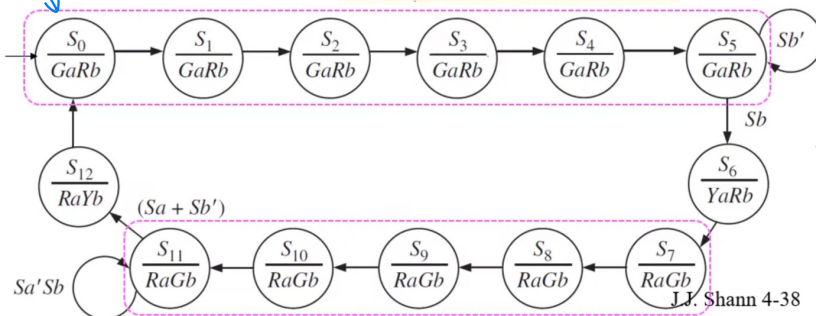

state diagram

J.J. Shann 4-38

# \* state table

present state	next state	(G <sub>a</sub> , Y <sub>a</sub> , R <sub>a</sub> , G <sub>b</sub> , Y <sub>b</sub> , R <sub>b</sub> )
$S_i (i=0 \sim 4)$	$S_{i+1}$	
$S_5$	$\begin{cases} S_b = 0 : S_5 \\ S_b = 1 : S_6 \end{cases}$	$G_a R_b$
$S_6$	$S_7$	$Y_a R_b$
$S_i (i=7 \sim 10)$	$S_{i+1}$	
$S_{11}$	$\begin{cases} S_a' S_b : S_{11} \\ S_a + S_b' : S_{12} \end{cases}$	$R_a G_b$
$S_{12}$	$S_0$	$R_a Y_b$
$S_i (i=13 \sim 15)$	$S_0$	0

\* We don't do state reduction since the states here also serve as a counter.

\* We use binary state assignment here.

$$S_0 \sim S_{12} \Rightarrow \underbrace{Q_A Q_B}_{msb} \underbrace{Q_C Q_D}_{lsb}$$

\* I'll deal with outputs first:

$$\left\{ \begin{array}{l} G_a = \sum m(0 \sim 5) \\ Y_a = S_6 = Q_A' Q_B Q_C Q_D' \\ R_a = \sum m(7 \sim 12) \\ G_b = \sum m(7 \sim 11) \\ Y_b = S_{12} = Q_A Q_B Q_C' Q_D' \\ R_b = \sum m(0 \sim 6) \end{array} \right.$$

$Q_C Q_D$ $Q_A Q_B$	00	01	11	10
00	1	1	1	1
01	0	1	0	0
11	0	0	0	0
10	0	0	0	0

$$G_A = Q_A' Q_B' + Q_A' Q_C' Q_D$$

$Q_A Q_B \backslash Q_C Q_D$	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	1	1	1	1
10	1	0	0	0

$$P_A = Q_A Q_B + Q_B Q_C Q_D + Q_A Q_C' Q_D'$$

$Q_A Q_B \backslash Q_C Q_D$	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	1	1	1	1
10	0	0	0	0

$$G_b = Q_A Q_B + Q_B Q_C Q_D$$

$Q_C Q_D$		$Q_A Q_B$			
		00	01	11	10
$Q_A Q_B$	00	1	1	1	1
	01	1	1	0	1
	11	0	0	0	0
	10	0	0	0	0

$$R_b = Q_A' Q_B' + Q_A' Q_C' + Q_A' Q_D' S_b$$

\* Next, I'll be dealing with next states  $Q^+$ :

present state				next state			
$Q_A$	$Q_B$	$Q_C$	$Q_D$	$Q_A^+$	$Q_B^+$	$Q_C^+$	$Q_D^+$
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	$S_b$	1	$S_b$	$S_b'$

0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	1	0	1	0
1	0	1	0	1	0	1	1
1	0	1	1	1	$(S_a' S_b)'$	$S_a' S_b$	$S_a' S_b$
1	1	0	0	0	0	0	0
1	1	0	1	0	0	0	0
1	1	1	0	0	0	0	0
1	1	1	1	0	0	0	0

$Q_C Q_D$	00	01	11	10
$Q_A Q_B$				
00	0	0	0	0
01	0	$S_b$	1	0
11	1	1	1	1
10	0	0	0	0

\*  $S_b$ ,  $S_a' S_b$  are MEVs

\* the result logic may not be the simplest as the MEVs are co-dependent

Solve for  $Q_A^*$

→ setting all MEVs to 0

$$Q_A^+ = (Q_A Q_B + Q_B Q_C Q_D)$$

$$+ S_b (Q_A Q_B + Q_B Q_D)$$

$Q_C Q_D \backslash Q_A Q_B$	00	01	11	10
00	0	0	1	0
01	1	1	0	1
11	0	0	$(S_a' S_b')$	0
10	0	0	0	0

Solve for  $Q_B^+$

$$Q_B^+ = (Q_A' Q_B Q_C' + Q_A' Q_B' Q_C Q_D$$

$$+ Q_A' Q_B Q_C Q_D' + Q_A Q_B Q_C Q_D)$$

$$+ S_a' S_b (0)$$



$Q_A Q_B \backslash Q_C Q_D$				
	00	01	11	10
00	0	1	0	1
01	0	$S_b$	0	1
11	0	1	$S_a' S_b$	1
10	0	0	0	0

Solve for  $Q_c^+$

$$\begin{aligned}
 Q_c^+ = & (Q_A' Q_C' Q_D + Q_B Q_C' Q_D \\
 & + Q_A' Q_C Q_D' + Q_B Q_C Q_D') \\
 & + S_b (Q_B Q_C' Q_D) \\
 & + S_a' S_b (Q_A Q_B Q_D)
 \end{aligned}$$

$Q_A Q_B \backslash Q_C Q_D$				
	00	01	11	10
00	1	0	0	1
01	1	$S_b'$	0	1
11	1	0	$S_a' S_b$	1
10	0	0	0	0

Solve for  $Q_D^+$

$$Q_D^+ = (Q_A' Q_D' + Q_B Q_D' + Q_A' Q_B Q_C') \\ + S_b(0)$$

$$+ S_A' S_b (Q_A' Q_B Q_D + Q_A Q_B Q_C)$$