

# 4.6 Scoreboard and Controller

## Scoreboard


### ■ Problem description:

- design a simple scoreboard, which can display scores from 0 to 99 (decimal).
- Inputs: a reset signal (*rst*) and control signals to increment (*inc*) or decrement (*dec*) the score
  - > The 2-digit decimal count gets +1 if *inc* signal is true and is -1 if *dec* signal is true.
  - > If *inc* and *dec* are true simultaneously, no action occur.
  - > **The reset button (*rst*) must be pressed for 5 consecutive cycles in order to erase the scoreboard.**
- The current count is displayed on 7-segment displays.

J.J. Shann 4-53


## Data Path

### ■ Block diagram of the scoreboard:

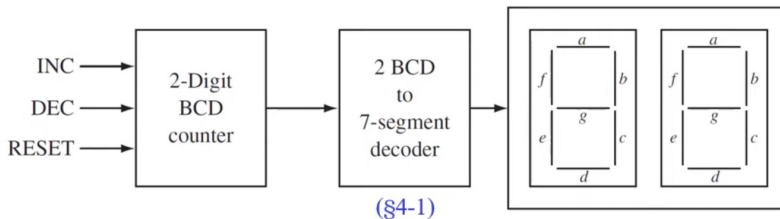


- True reset should happen only after pressing reset for 5 clock cycles
  - ⇒ Use a **3-bit reset counter** called *rescnt*.

J.J. Shann 4-54

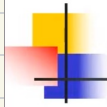

# Controller

## ■ State graph for scoreboard:

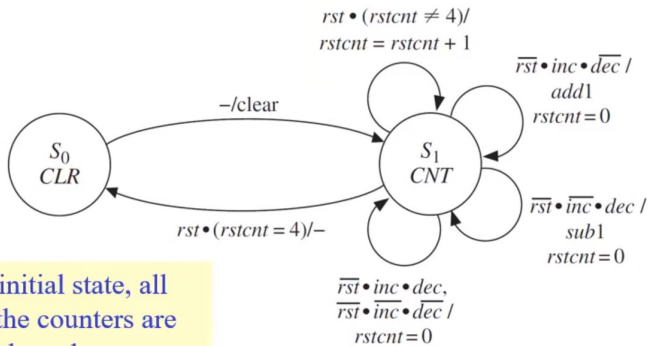

\*  $S_0$ : initial state, all the counters are cleared

J.J. Shann 4-55

- A system rst is added to my design
- $\text{rst} \rightarrow \text{erase}$   
 $\text{rstcnt} \rightarrow \text{erasecnt}$