

8.4 Built-in Primitives

1 Introduction

- built-in primitives: provide gate and switch level modeling facility.
 - predefined logic gate primitives: 14
 - predefined switch primitives: 12
- advantages of modeling at gate or switch level
 - synthesis tools can easily map it to the desired circuitry since gates provide a very close 1-1 mapping b/w ckt & model.
 - There are primitives such as the bidirectional transfer gate that cannot be otherwise modeled using dataflow or behavioral level.

Built-in Primitives in Verilog

* Output port(s) first followed by input(s).

Gate-level Primitive	Type
and, nand, nor, or, xnor, xor	n-input gates (1 output)
buf, not	n-output gates (1 input)
bufif0, bufif1, notif0, notif1	Three-state gates

Switch-level Primitive	Type
pulldown, pullup	Pull gates; resistor
cmos, nmos, pmos, rcmos, rnmos, rpmos	MOS switches
rtran, rtranif0, rtranif1, tran, transif0, tranif1	Bidirectional switches

8-34

Example: Array of Tristate Buffers

- Model an array of four inverting tristate buffers using built-in primitive:

```
module tri_driver (in, out, tri_en);
```

```
  input [3:0] in;
```

```
  output [3:0] out;
```

```
  input tri_en;
```

* *Output* first followed by *inputs, control* last.

```
  bufif0 buf_array[3:0] (out, in, tri_en); // array of tristate buffers
```

```
endmodule
```

- buf_array[3:0] is used as instance name and is indexed.
- Statement could be replaced using instance names that are not indexed:

```
  bufif0 buf_array3 (out[3], in[3], tri_en);
```

```
  bufif0 buf_array2 (out[2], in[2], tri_en);
```


```
  bufif0 buf_array1 (out[1], in[1], tri_en);
```

```
  bufif0 buf_array0 (out[0], in[0], tri_en);
```

J.J. Shann 8-37



Example

 

```
module tri_buffer (a,b,c,d,f);  
  input a,b,c,d;  
  output f;  
  
  bufif1 buf_one (f,a,b);  
  bufif1 buf_two (f,c,d);  
endmodule
```

* **Output** first followed by **inputs**, **control** last.

J.J. Shann 8-38

- delay specification for built-in primitives
 - built-in primitives can have an optional delay specification
 - delay specification can contain up to 3 delay values, depending on the gate.
 - 1st delay: transition to rise delay
(transition to 1)
 - 2nd delay: transition to fall delay
(transition to 0)

- 3rd delay: transition to high impedance delay
(turn off delay)



Examples: Primitives w/ Delays

- Examples: primitives with delays:
 - **and** # (10) a1 (out, in1, in2);
// only one delay so rise delay = 10
 - **and** # (10,12) a2 (out, in1, in2);
// rise delay = 10 and fall delay = 12
 - **bufif0** # (10,12,11) b3 (out, in, ctrl);
// rise, fall, and turn-off delays