

6.1 Implementing Functions in FPGAs

1 Issues Related to Implementing Designs in FPGAs

- hand-mapping simple designs into FPGA building blocks to illustrate tradeoffs arising from the structure of the basic FPGA building blocks.
- Shannon's expansion for decomposition of large functions into smaller functions.
- One-hot state assignment method for FPGA-like technology
- Design flow, synthesis, mapping - and placement issues
- features of some commercial FPGAs


2 Implementing Functions in FPGAs

- Many modern FPGAs use a 4-input look-up table (LUT4) as basic building blocks.
- It takes $2^4 = 16$ bits of SRAM to realize LUT4 using SRAM technology.


Ex. 4×1 MUX

 Example: 4-to-1 MUX

- Design a 4-to-1 multiplexer using an FPGA with *look-up tables (LUTs)* and *flip-flops*.
 - Each building block contains two 4-variable function generators, and two flip-flops.



A 4-to-1 multiplexer

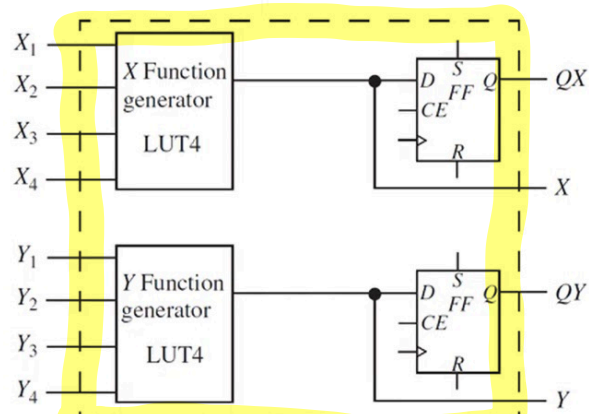

A building block of the FPGA 6-8

<Ans.>


- For the 4-to-1 MUX:


- Inputs: 6; multiplexer inputs $I_0, I_1, I_2,$ and I_3 and multiplexer selects S_1 and S_0
- Output equation:

$$\begin{aligned} M &= S_1' S_0' I_0 + S_1' S_0 I_1 + S_1 S_0' I_2 + S_1 S_0 I_3 \\ &= S_1' (S_0' I_0 + S_0 I_1) + S_1 (S_0' I_2 + S_0 I_3) \end{aligned}$$

- Decompose into three 2-to-1 MUXs:
 
$$\begin{aligned} M_1 &= S_0' I_0 + S_0 I_1 \\ M_2 &= S_0' I_2 + S_0 I_3 \\ M &= S_1' M_1 + S_1 M_2 \end{aligned}$$



 


$$M_1 = S_0'I_0 + S_0I_1$$

$$M_2 = S_0'I_2 + S_0I_3$$

$$M = S_1'M_1 + S_1M_2$$

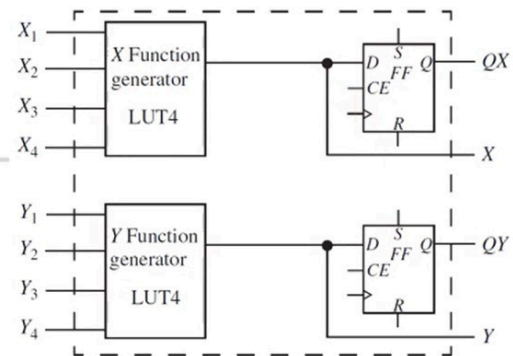- Two logic blocks will be required to implement a 4-to-1 MUX.



A building block of the FPGA

- The functions generated by the 1st logic block:

$$X = M_1 = S_0'I_0 + S_0I_1$$

$$Y = M_2 = S_0'I_2 + S_0I_3$$

- Only half of the 2nd logic block is used:

$$X = M = S_1'M_1 + S_1M_2$$


- The flip-flops are unused in this design.

6-10

$$M_1 = S_0'I_0 + S_0I_1$$

$$M_2 = S_0'I_2 + S_0I_3$$

$$M = S_1'M_1 + S_1M_2$$

 

- The contents of the look-up tables:

- Assumption: X_1 and Y_1 are the LSBs, and X_4 and Y_4 are the MSBs of the LUT addresses.

- Truth table of LUT-M1:
a 2-to-1 MUX

- The contents of LUT-M1:

LUT-M1– 0, 1, 0, 1, 0, 0, 1, 1,
0, 1, 0, 1, 0, 0, 1, 1

Inputs				Output
X_4	$X_3 (S_0)$	$X_2 (I_1)$	$X_1 (I_0)$	X
x	0	0	0	0
x	0	0	1	1
x	0	1	0	0
x	0	1	1	1
x	1	0	0	0
x	1	0	1	0
x	1	1	0	1
x	1	1	1	1


- LUT-M2, LUT-M: the same as LUT-M1




Implementing Functions in FPGAs

- Some FPGAs provide two 4-variable function generators and a method to combine the output of the two function generators.

— E.g.:

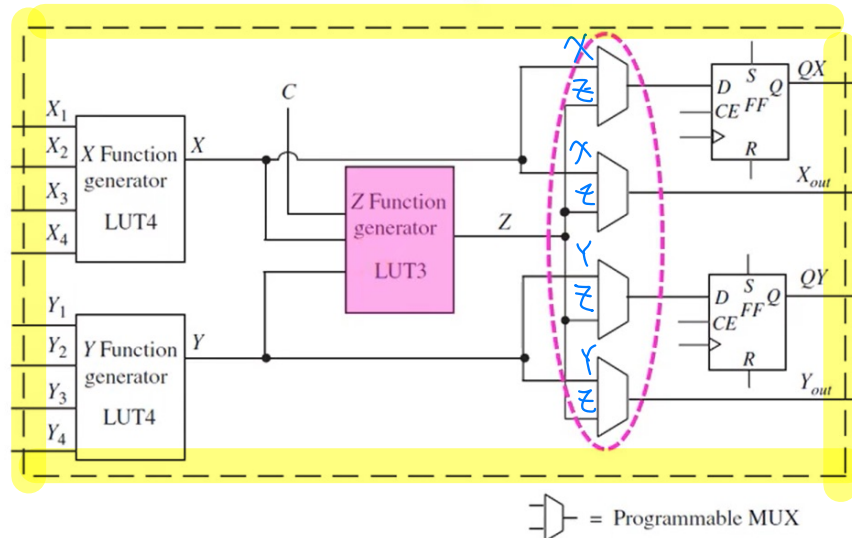


i-13

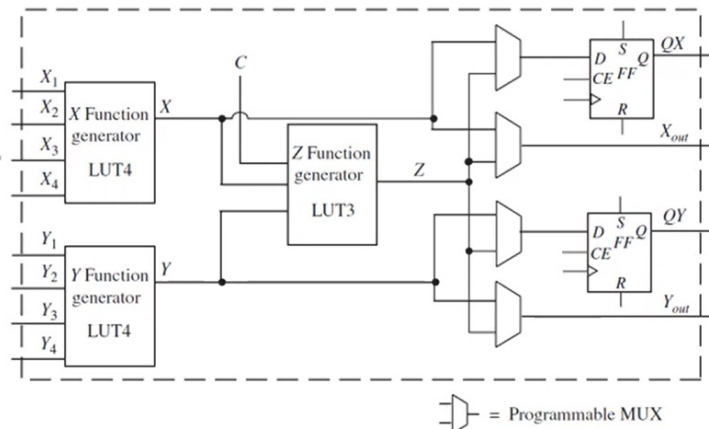


- The programmable logic block has **nine** logic inputs:
 $X_1, X_2, X_3, X_4, Y_1, Y_2, Y_3, Y_4$, and C
- It can generate **two** independent functions of **four** variables, $f_1(X_1, X_2, X_3, X_4)$ and $f_2(Y_1, Y_2, Y_3, Y_4)$, and a function Z which depends on f_1, f_2 , and C , $Z(f_1, f_2, C)$.
- It can generate any function of **five** variables in the form $Z = f_1(F_1, F_2, F_3, F_4) \cdot C' + f_2(F_1, F_2, F_3, F_4) \cdot C$, and can generate some functions of 6 to 9 variables.

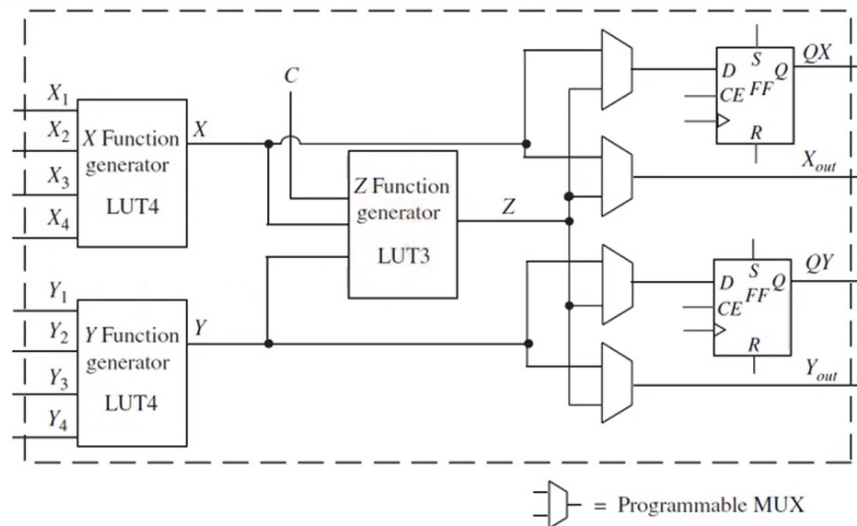Example: 4-to-1 MUX

- Consider the implementation of a 4-to-1 MUX using a single logic block of this FPGA.



6-15

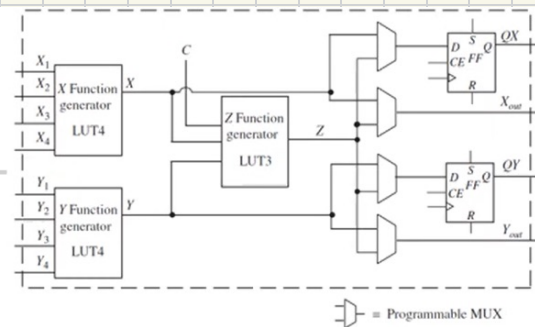

- X function generator (LUT4) generates the function: $F_1 = S_1'S_0'I_0 + S_1'S_0I_1$
- Y function generator (LUT4) generates the function: $F_2 = S_1S_0'I_2 + S_1S_0I_3$
- Z function generator (LUT3) performs an OR function of the F_1 and F_2 functions: $Z = F_1 + F_2$

- * In this case, the C input is not required.
- * Often, there are many ways to map the same design.
- * It is very expensive to create multiplexers using LUTs.




Resources in FPGAs

■ SRAM cells:

- 3-input function generator (LUT3): 8 SRAM cells
- 4-input function generators (LUT4): 16 SRAM cells

■ E.g.:

- 40 memory cells

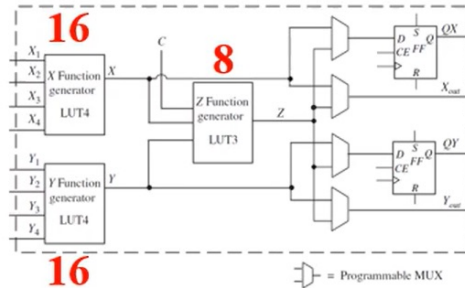


- When the *programmable logic block* of an FPGA is a large unit w/ ability to realize a fairly complex multivariable function, it is possible that a large part of each logic block may go unused.


J.J. Shann 6-19

Ex. Shift Register



Example

 

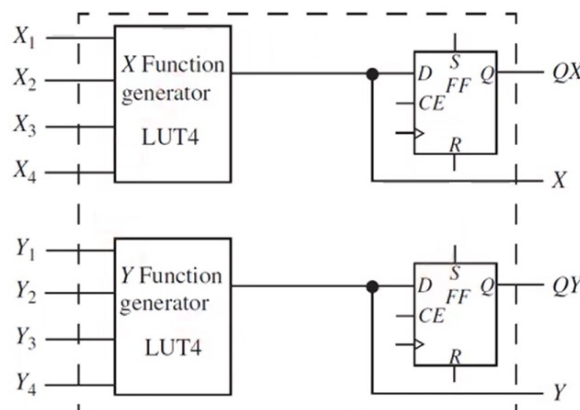- Design a 4-bit *circular shift register*, i.e., a *ring counter*, in an FPGA whose building block is shown below.



J.J. Shann 6-20

  

- * The 4-variable function generators are largely unused in this example.
- * Even if a function generator is used for a single variable function the rest of the function generator cannot be used for anything else.


Shann 6-21



Ex. 3×8 decoder

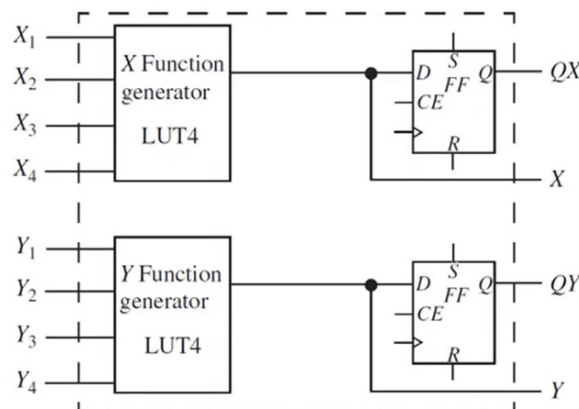
Example: 3-to-8 Decoder

- How many programmable logic blocks similar to the one below will be required to create a 3-to-8 decoder?



(Review)

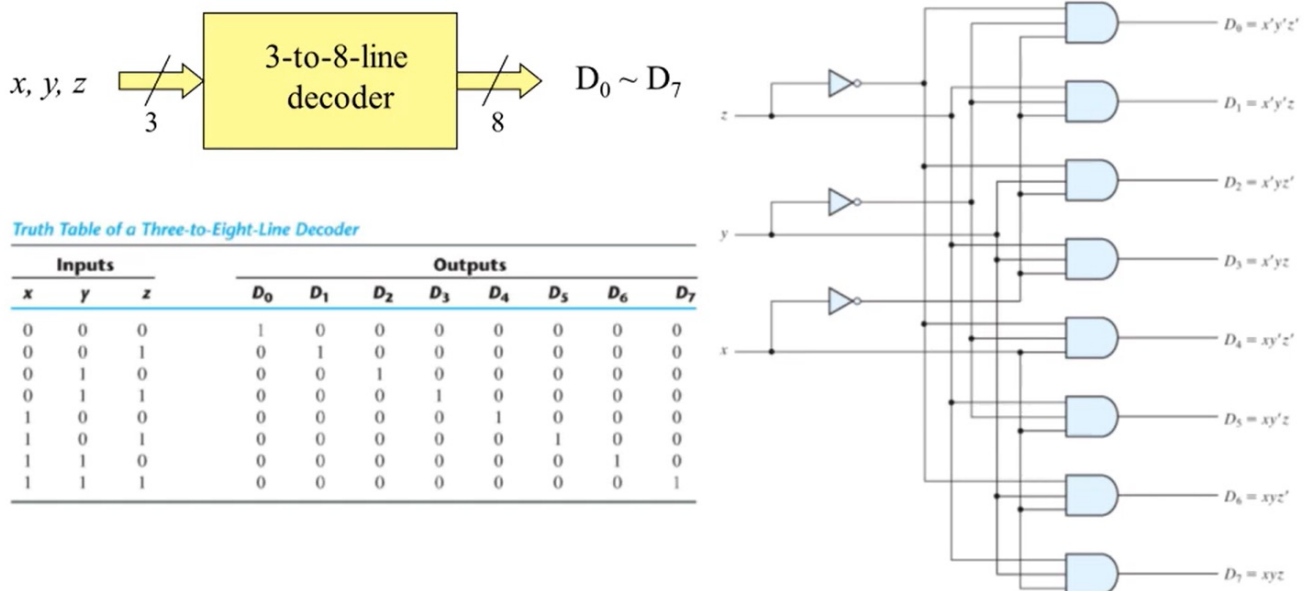■ 3-to-8 (line) decoder: active-HIGH outputs




J.J. Shann 6-23

<Ans.>

■ Answer: Four.

- A 3-to-8 decoder has three inputs and eight outputs.
 - Each output will need a 3-variable function generator.
 - Since what is available in the logic block is a 4-variable function generator, one will have to use one such function generator to create one output.
- ⇒ Eight function generators will be required to create a 3-to-8 decoder.
- ⇒ Four programmable logic blocks will be required to create a 3-to-8 decoder. (One logic block can generate two outputs.)

 

- different building blocks of FPGAs
 - Some FPGAs use muxes and gates as basic building blocks.
 - Some FPGAs (e.g. Xilinx) provide LUTs and muxes.
 - The mapping software looks at the resources available in the target technology (i.e. the specific FPGA that is used) and translates the design into the available building blocks.