 


### 3.3 CPLDs


#### 1 What are CPLDs?

- a number of PAL / PLA - like logic blocks
- a programmable interconnect matrix
  - crossbar - like switch
  - $N \times M$  crossbar switch
    - Each of the  $N$  input lines can be connected to the  $M$  output lines **simultaneously**.
    - Building the switches is expensive but results in predictable timing.
- storage elements : FFs

Exl. Xilinx CoolRunner




## ■ Function block & macrocell:

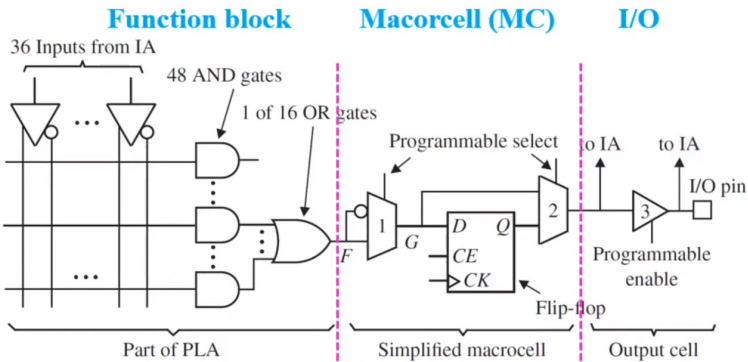

Ex2. Mealy Seq Ckt

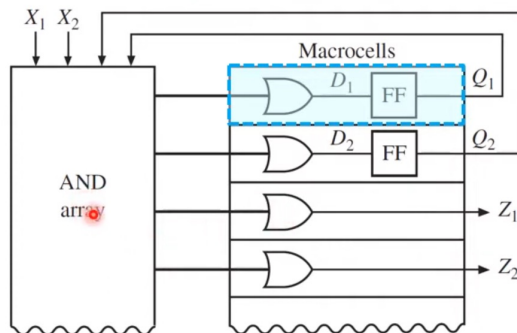
## Example: Mealy seq ckt

- A Mealy seq ckt w/  
2 inputs, 2 outputs, and 2 flip-flops:


 
## Example: N-Bit Parallel Adder w/ Accumulator


- Implement an  $n$ -bit parallel adder w/ an accumulator in a CPLD:



J.J. Shann 3-53

<Ans.>

- 3 bits of the adder:

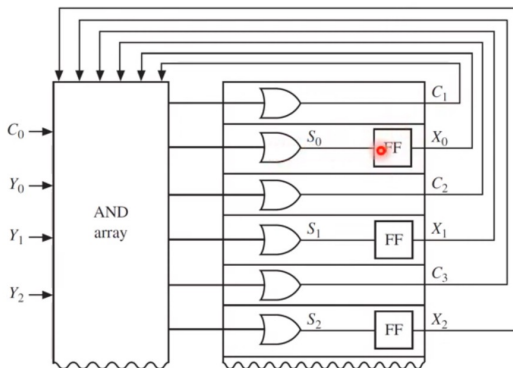

For each accumulator f-f:

$$D_i = X_i^+ = S_i \\ = X_i \oplus Y_i \oplus C_i$$

For carry:

$$C_{i+1} = X_i Y_i + X_i C_i + Y_i C_i$$

J.J. Shann 3-54