

5.3 Realization of SM Chart

- state reduction:
 - difficult to eliminate redundant states in an SM chart as the chart is usually **incompletely specified**.
 - combining states may make the SM chart more difficult to interpret.
- state assignment
 - The best way of making the assignment depends on how the SM chart is realized.
 - gates & FFs (or equivalent PLD realization): follow the guidelines for state assignment given in 1-7.
 - programmable gate array (e.g. FPGA):
 - one-hot encoding** may be best

↓

FPGAs are rich in FFs but poor in combinational paths

- output and next-state equations
 - after the state assignment has been made, output & state equations can be read directly from the SM chart.
 - procedure for deriving the next state equations for a FF Q from the SM chart
 1. identify all states in which $Q = 1$.
 2. For each of these states, find all link paths that lead to this state.
 3. For each of these link paths, find a term that is 1 when the link path is followed.
 - for a link path from S_i to S_j , the term will be 1 if the machine is in state S_i and the conditions for exiting to S_j are met.
 4. The expression for Q^+ is formed by

ORing together the terms in step 3.



Example

- Derive the *output & next state equations* from the SM chart.


- Output equations:

$$Z_a = A'B'$$

$$Z_b = A'B$$

$$Z_c = AB$$

$$Z_1 = ABX'$$

 

J.J. Shann 5-76



- Nest state equations:


$$A^+ = \text{link 2 link 3 } A'BX + \text{link 3 } ABX$$

$$= \dots$$


$$B^+ = \text{link 1 link 2 } A'B'X + \text{link 2 } A'BX$$

$$+ \text{link 3 } ABX$$

$$= \dots$$

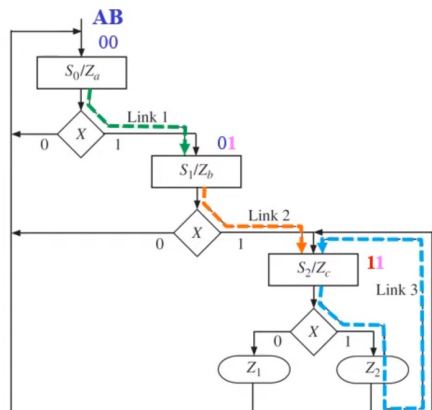

J.J. Shann 5-77

 

Implementation 1

■ SM chart:

- trace *link paths* on the SM chart and then simplify the resulting equations

- Output equations:

$$Load = A'B'St$$

$$Sh = A'BM' + AB'$$

$$Ad = A'BM$$


$$Done = AB$$

- Next-state equations:

$$A^+ = A'BM + A'BM'K + AB'K = A'B(M + K) + AB'K$$

$$B^+ =$$

=

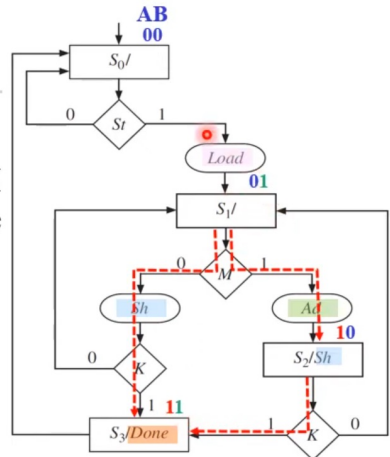

J.J. Shann 5-81



■ SM chart:

- trace *link paths* on the SM chart and then simplify the resulting equations

- Output equations:

$$Load = A'B'St$$

$$Sh = A'BM' + AB'$$

$$Ad = A'BM$$


$$Done = AB$$

- Next-state equations:

$$A^+ = A'BM'K + A'BM + AB'K = A'B(M + K) + AB'K$$

$$B^+ = A'B'St + A'BM'K' + AB'K' + A'BM'K + AB'K$$

$$= A'B'St + A'BM' + AB'$$

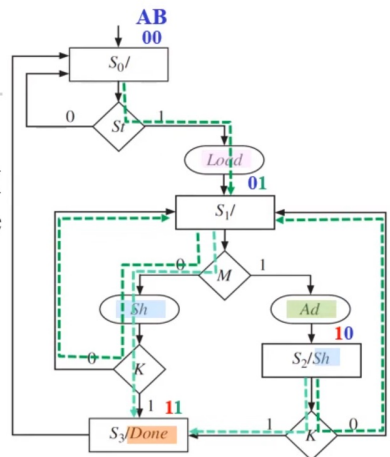


J.J. Shann 5-82



Implementation 2

State transition table:

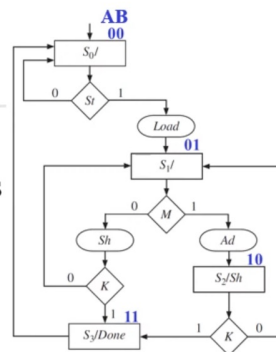- Each **row** in the table corresponds to one **link path** in the SM chart.
- The outputs for each row can be filled in by tracing the corresponding link paths on the SM chart.



	Present state		Inputs			Next state		Outputs				
	A	B	St	M	K	A ⁺	B ⁺	Load	Sh	Ad	Done	
S ₀	0	0	0	—	—	0	0	0	0	0	0	
	0	0	1	—	—	0	1	1	0	0	0	
S ₁	0	1	—	0	0	0	1	0	1	0	0	
	0	1	—	0	1	1	1	0	1	0	0	
	0	1	—	1	—	1	0	0	0	1	0	
S ₂	1	0	—	—	0	0	1	0	1	0	0	
	1	0	—	—	1	1	1	0	1	0	0	
S ₃	1	1	—	—	—	0	0	0	0	0	1	




Implement

the multiplier controller w/ ROM:

- Determine the size of the ROM: 32×6
 - 5 different inputs to the comb ckt (A , B , St , M , and K)
 \Rightarrow 32 entries.
 - Comb ckt should generate six signals
 \Rightarrow Each entry has to be 6 bits wide.
- \Rightarrow This design can be implemented using a 32×6 ROM and two D flip-flops.

	A	B	St	M	K	A ⁺	B ⁺	Load	Sh	Ad	Done
S ₀	0	0	0	—	—	0	0	0	0	0	0
	0	0	1	—	—	0	1	1	0	0	0
S ₁	0	1	—	0	0	0	1	0	1	0	0
	0	1	—	0	1	1	1	0	1	0	0
	0	1	—	1	—	1	0	0	0	1	0
S ₂	1	0	—	—	0	0	1	0	1	0	0
	1	0	—	—	1	1	1	0	1	0	0
S ₃	1	1	—	—	—	0	0	0	0	0	1

 


- If a ROM is used, the table must be expanded to $2^5 = 32$ rows as there are 5 inputs.
 - Dashes must be replaced with all combinations of 0s and 1s. \Rightarrow If a row has n dashes, it must be replaced by 2^n rows.

A	B	St	M	K	A ⁺	B ⁺	Ld	Sh	Ad	Done
...										
0	1	–	1	–	1	0	0	0	1	0
...										


0	1	0	1	0	1	0	0	0	1	0
0	1	0	1	1	1	0	0	0	1	0
0	1	1	1	0	1	0	0	0	1	0
0	1	1	1	1	1	0	0	0	1	0

5-85

 

- Standard ROM (LUT) implementation of the multiplier: original SM chart
 - 4 states \Rightarrow 2 flip-flops, 2 next state equations
 - 3 inputs: St, M, K
 - 4 outputs: *Load*, *Sh*, *Ad*, *Done*
 - ROM size: 32×6

A	B	St	M	K	A ⁺	B ⁺	Ld	Sh	Ad	Done
...										

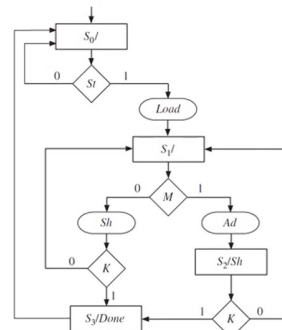

J.J. Shann 5-138