

## 4.9 Shift and Add Multiplier



### A Shift-and-Add Multiplier

- Problem description:
  - Design a multiplier for **unsigned** binary numbers.
  - Form the *product*  $A \times B$ 
    - the 1<sup>st</sup> operand ( $A$ ): *multiplicand*,
    - the 2<sup>nd</sup> operand ( $B$ ): *multiplier*.
- *Serial-parallel multiplier*:
  - The multiplier bits are processed serially, but addition takes place in parallel.

J.J. Shann 4-78



### Multiplication for Unsigned Binary Numbers

- Multiplication for *unsigned* binary numbers:


– E.g.:

Multiplicand	→	1 1 0 1	(13)
Multiplier	→	1 0 1 1	(11)
		1 1 0 1	
		1 1 0 1	
Partial products		1 0 0 1 1 1	
		0 0 0 0	
		1 0 0 1 1 1	
		1 1 0 1	
		1 0 0 0 1 1 1 1	(143)


- Binary multiplication requires only *shifting* and *adding*.
- Each *partial product* is either *the multiplicand shifted over by the appropriate # of places* or *zero*.
- Each new partial product is added in as soon as it is formed.

4-79

## Block Diagram of 4×4 Multiplier

 

 - Block diagram for binary multiplier of two 4-bit numbers:



*St*: start signal; *M*: current multiplier bit

*Load*: load multiplier into the lower 4 bits of ACC and clear the upper 5 bits of ACC

*Sh*: shift signal, shift all 9 bits of ACC to the **right** by the next clock pulse

*Ad*: add signal, transfers the adder outputs to the upper 5 bits of ACC by the next clock pulse

*Done*: done signal

*St*: start signal


*M*: current multiplier bit

*Load*: load multiplier into ACC[3:0] and clear the ACC[8:4]

*Sh*: shift signal, shift ACC[8:0] to the **right** by the next clock pulse

*Ad*: add signal, transfers the adder outputs to the ACC[8:4] by the next clock pulse

*Done*: done signal

 

- a 4-bit multiplicand
- a 4-bit multiplier register
- a 4-bit full adder
- an 8-bit register for the product
  - The product register serves as an accumulator to accumulate the sum of the **partial product**.
  - The contents of the product register will be **shift** to the **right** each time before added with the multiplicand.
- an extra bit at the left end of the product register
  - temporarily stores any **carry** generated by the adder


## Example

### ■ Multiply $13_{10}$ by $11_{10}$ in binary:

– the location of the bits in the regs at clock time:

initial contents of product register	0 0 0 0 0   1 0 1 1	← $M(11)$
(add multiplicand since $M = 1$ )	1 1 0 1	(13)
after addition	0 1 1 0 1   1 0 1 1	
after shift	0 0 1 1 0 1   1 0 1	← $M$
(add multiplicand since $M = 1$ )	1 1 0 1	
after addition	1 0 0 1 1 1   1 0 1	
after shift	0 1 0 0 1 1   1 1 0	← $M$
(skip addition since $M = 0$ )		
after shift	0 0 1 0 0 1 1   1	← $M$
(add multiplicand since $M = 1$ )	1 1 0 1	
after addition	1 0 0 0 1 1 1 1	
after shift (final answer)	0 1 0 0 0 1 1 1 1	(143)

 dividing line between product and multiplier



4-82

## First Controller Design


## State Graph of 4x4 Multiplier

### ■ State graph for control ckt:


– designed to output the proper sequence of *add* and *shift* signals

\* The max # of clock cycles needed for a multiply is 10.

 ←  $2(n+1)$   
where  
 $n = \#$   
(bits to add)



 **St**: start signal  
**M**: current multiplier bit  
**Load**: load multiplier into ACC[3:0] and clear the ACC[8:4]  
**Sh**: shift signal, shift ACC[8:0] to the right by the next clock pulse  
**Ad**: add signal, transfers the adder outputs to the ACC[8:4] by the next clock pulse  
**Done**: done signal



4-83

↖ this state machine design is bad when # (bits to add) is large

## Second Controller Design



### SM Chart

#### ■ SM chart for control the binary multiplier:

- The **add-shift control** generates the required sequence of add and shift signals.
- The **counter** counts the # of shifts and outputs  $K = 1$  just before the last shift occurs.

