

7.2.1 FLP Multiplier

Hardware

- * Use 4-bit fractions and 4-bit exponents.
- * Negative numbers are represented in 2's complement.

■ Major components of the FP multiplier:


- **Exponent adder:** uses a 5-bit full adder for the 2's complement exponents
- **Fraction multiplier:** implements a *shift* and *add* multiplier algorithm for the 2's complement fractions (Refer to the faster multiplier in §4-10)
- **Major control unit:** provides the signals to perform the appropriate ops of *right shifting*, *left shifting*, *exponent incrementing/decrementing*, and so forth.

7-36

Exponent Adder

■ Exponent adder:

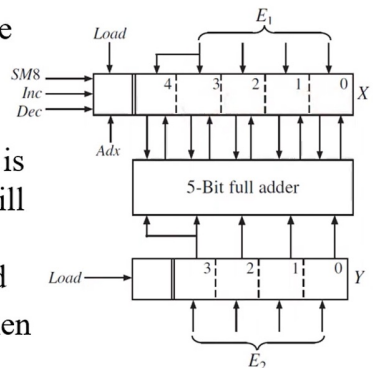- uses a 5-bit full adder for the 2's complement exponents
- **Load, Adx**
- **Inc, Dec:** when the fraction is normalized, the exponent will have to be correspondingly incremented or decremented
- **SM8:** in the special case when **product is 0**, the register should be set to the value **1000**




7-37

Fraction Multiplier

■ Fraction multiplier:

- implements a *shift* and *add* multiplier algorithm for the 2's complement fractions (faster multiplier in §4-10)
- Multiply 3 bits plus sign by 3 bits plus sign.
 \Rightarrow The result will be 6 bits plus sign, i.e., the lower 3 bits of A concatenated w/ B.
- **Multiply control:** generates appropriate shift and add signals depending on the multiplier bits
 - The controller is *linked* into the main controller: **Adx**, **Mdone**
linked state machine
(similar to procedure call)

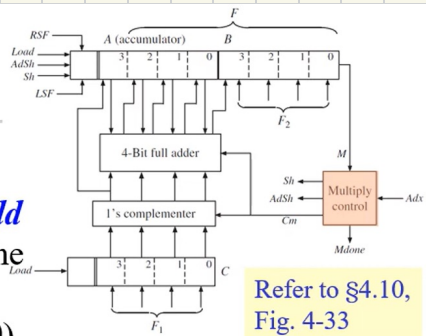


Refer to §4.10, Fig. 4-33

7-38

Major Control Unit

■ Main control unit:


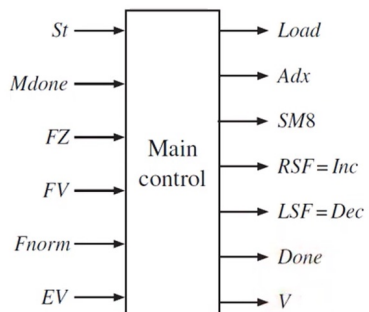
- provides the signals to perform the appropriate operations of *right shifting*, *left shifting*, *exponent +1/-1*,



7-39

SM Chart of Main Controller

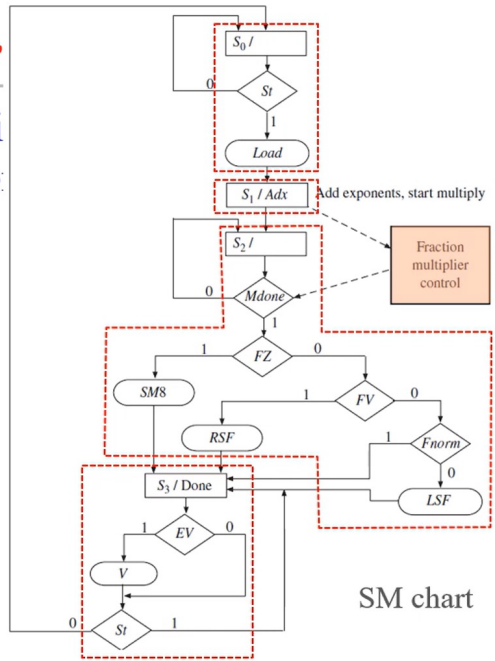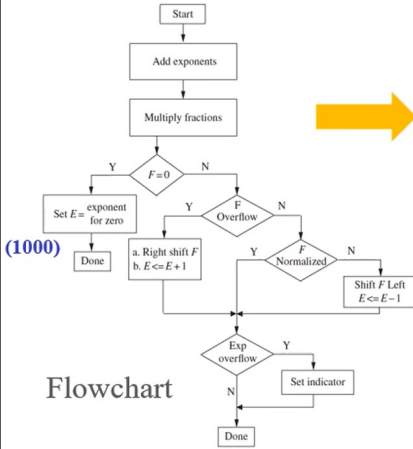■ SM chart for floating point multiplication



Input signals


- **St**: Start the floating-point multiplication.
- **Mdone**: Fraction multiply is done.
- **FZ**: Fraction is zero.
- **FV**: Fraction overflow (fraction is too big).
- **Fnorm**: F is normalized.
- **EV**: Exponent overflow.

Control signals

- **Load**: Load F_1, E_1, F_2, E_2 into the appropriate registers; also clear A.
- **Adx**: Add exponents; also starts the fraction multiplier.
- **SM8**: Set exponent to -8 (1000, to handle special case of 0).
- **RSF**: Shift fraction right; also increment E.
- **LSF**: Shift fraction left; also decrement E.

Output signals



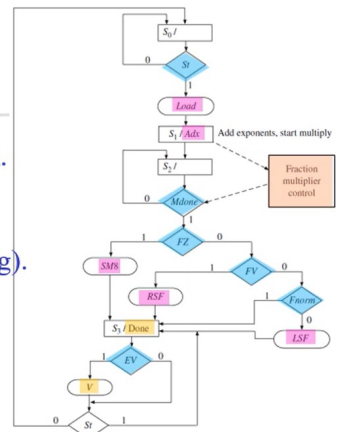
- **V**: Overflow indicator.
- **Done**: Floating-point multiplication is complete.



State Graph of Multiplier Control

■ State graph for multiplier control:

§4.10
Fig. 4-34

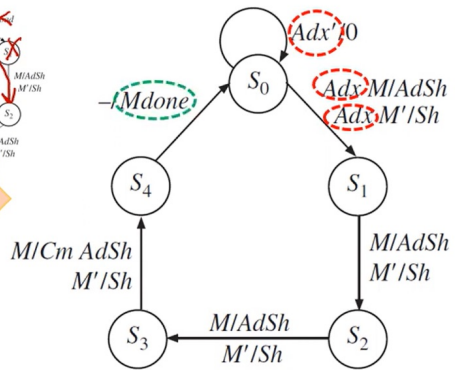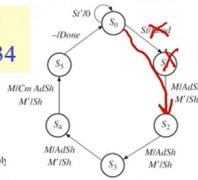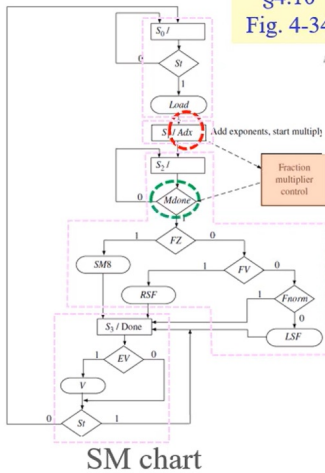

State graph

* "Load" has been done in
main controller!

7-43