

## 8.5 User Defined Primitives

### 1 Introduction

- multiple input ports, one output port
- define its functionality in
  - { truth table : combinational
  - state fable : sequential
- can be instantiated as built-in primitives.
- ports :
  - bidirectional inout ports are not allowed in UDPs.
  - No vector ports are allowed.
  - tristate / high-impedance state (Z) is not allowed. (0, 1, x are allowed)
    - Z inputs are interpreted as x
  - In seq UDPs, the output always has the same value as the internal state.

## Form of UDPs

### ■ Basic form of a UDP: *truth table*

**primitive** primitive\_name (**output**, input, input, ... );

**output** terminal\_declaration;

**input** terminal\_declaration;

**reg** output\_terminal;

**initial** output\_terminal = logic\_value;

**table**

table\_entry; // inputs : output ;

{table\_entry;}

**endtable**

**endprimitive**

8-46

Ex. UDP for 2x1 MUX

## Example

### ■ UDP for 2-to-1 MUX:

- The input combination 0xx is not specified.
- If this combination occurs during simulation, the value of output port *F* will become x.

\* x: unknown

```
primitive mux1 (F, A, I0, I1);
  output F;
  input A, I0, I1; //A is the select input
```

//	A	I0	I1	F
0	1	0	:	1;
0	1	1	:	1;
0	1	x	:	1;
0	0	0	:	0;
0	0	1	:	0;
0	0	x	:	0;
1	0	1	:	1;
1	1	1	:	1;
1	x	1	:	1;
1	0	0	:	0;
1	1	0	:	0;
1	x	0	:	0;
x	0	0	:	0;
x	1	1	:	1;

**endtable**

**endprimitive**

8-48

## Example: UDP for 2-to-1 MUX

### ■ UDP for a 2-to-1 multiplexer using “?” :

- The ? means that signal listed with it can take the values of 0,1, or x.

```
primitive mux2 (F, A, I0, I1);
```

```
output F;
```

```
input A, I0, I1;
```

```
table
```

//	A	I0	I1	F
	0	1	?	1;
	0	0	?	0;
	1	?	1	1;
	1	?	0	0;
x	0	0		0;
x	1	1		1;

```
endtable
```

```
endprimitive
```

8-49

### 3 Sequential UDPs

- Outputs must have the same state as the internal state.
- The output must be defined as reg.
- Can model both edge-sensitive and level-sensitive behavior.

- edge-sensitive behavior can be represented in tabular form by listing the value before and after the edge.

$$\begin{cases} 01 : \text{rising edge} \\ 10 : \text{falling edge} \end{cases}$$

- each table entry  
inputs : present state : outputs

- If level-sensitive behavior such as async set and reset are in a table along w/ edge-sensitive behavior for data, the level-sensitive behavior should be listed before the edge-sensitive behavior.

# Example: Sequential UDP for a D Flip-Flop

Table entry

inputs : present state : output;

## ■ Sequential UDP for a D flip-flop:

primitive DFF (Q, CLK, D);

output Q;

input CLK, D;

reg Q;

table

```
// CLK, D, Q, Q+
(01) 0 : ? : 0;
(01) 1 : ? : 1;
(0?) 1 : 1 : 1;
(?0) ? : ? : -;
? (??) : ? : -;
```

endtable

endprimitive

\* “-”: the output should not change for any of the circumstances covered by that line.

\* “?”: can take the values of 0, 1, or x

//rising edge with input 0

//rising edge with input 1

//Present state 1, either rising edge or steady clock

//Falling edge or steady clock, no change in output

//Steady clock, ignore inputs, no change in output

\* Make the truth table as unambiguous as possible!